

EE105 Lab Experiments

Prelab 8: Multi-stage Amplifiers

Name:

Lab Section:

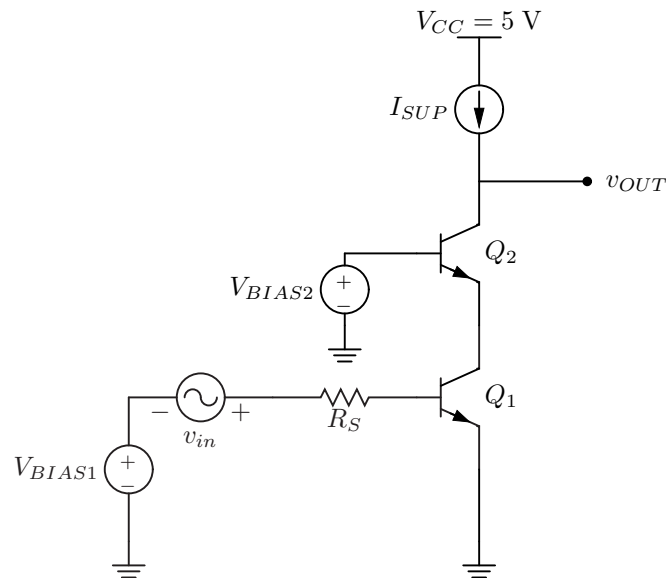


Figure 1: Cascode amplifier with ideal current source

1. The cascode in Figure 1 is biased by an ideal current source. Let $R_S = 51 \, \Omega$, $I_S = 1 \times 10^{-15} \, \text{A}$, $V_A = 100 \, \text{V}$, $\beta = 200$, $I_{SUP} = 1 \, \text{mA}$, $T = 300 \, \text{K}$, $v_{OUT,DC} = 3.5 \, \text{V}$, and $V_{BIAS2} = 2 \, \text{V}$. Calculate V_{BIAS1} to match these biasing conditions.

$V_{BIAS1} =$

2. What is the gain of this amplifier?

$A_v =$

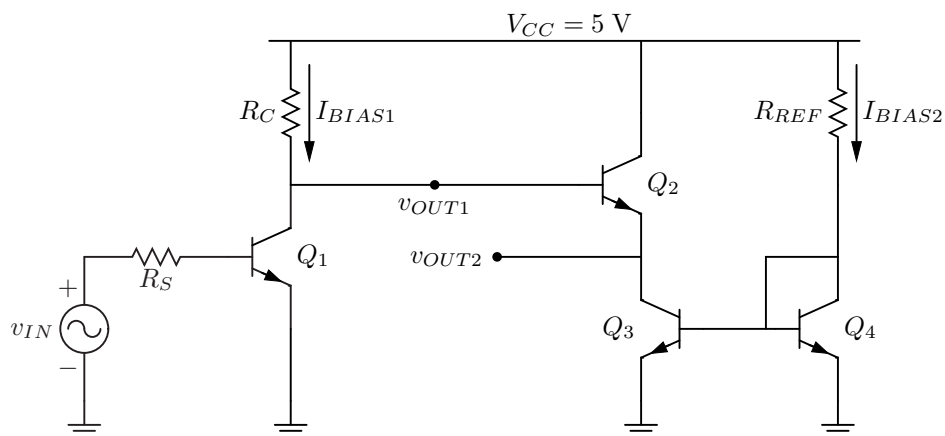


Figure 2: Multi-stage amplifier

3. Now construct a SPICE netlist for the multi-stage amplifier shown in Figure 2. Let $R_C = 10 \text{ k}\Omega$, $R_S = 51 \Omega$, and $R_{REF} = 200 \Omega$. Bias transistor Q_1 with $V_{BE1} = 560 \text{ mV}$. What is the small signal gain (A_{v1}) between v_{IN} and v_{OUT1} ? What is the small signal gain (A_{v2}) between v_{OUT1} and v_{OUT2} ? Using A_{v1} and A_{v2} , find the overall gain ($A_{v,tot}$) between v_{IN} and v_{OUT2} . Attach the SPICE netlist to the end of this prelab.

$A_{v1} =$

$A_{v2} =$

$A_{v,tot} =$