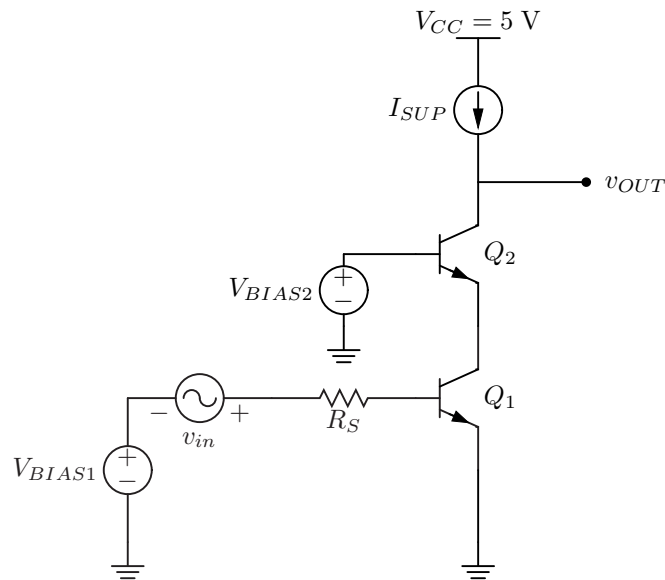


EE105 Lab Experiments

## Prelab 8: Multi-stage Amplifiers

Name:

Lab Section:




**Figure 1:** Cascode amplifier with ideal current source

1. The cascode in Figure 1 is biased by an ideal current source. Let  $R_S = 51 \, \Omega$ ,  $I_S = 1 \times 10^{-15} \, \text{A}$ ,  $V_A = 100 \, \text{V}$ ,  $\beta = 200$ ,  $I_{SUP} = 1 \, \text{mA}$ ,  $T = 300 \, \text{K}$ ,  $v_{OUT,DC} = 3.5 \, \text{V}$ , and  $V_{BIAS2} = 2 \, \text{V}$ . Calculate  $V_{BIAS1}$  to match these biasing conditions.

$V_{BIAS1} =$

2. What is the gain of this amplifier?

$A_v =$

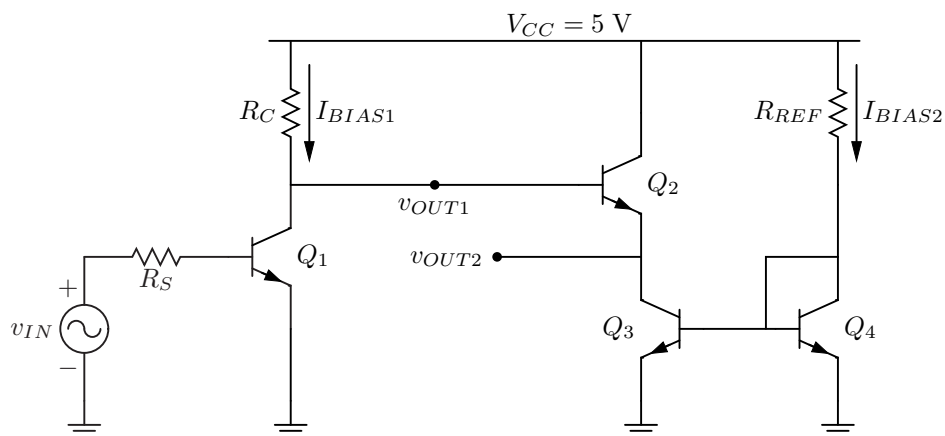

**Figure 2:** Multi-stage amplifier

3. Now construct a SPICE netlist for the multi-stage amplifier shown in Figure 2. Let  $R_C = 10 \text{ k}\Omega$ ,  $R_S = 51 \text{ k}\Omega$ , and  $R_{REF} = 200 \text{ }\Omega$ . Bias transistor  $Q_1$  with  $V_{BE1} = 560 \text{ mV}$ . What is the small signal gain ( $A_{v1}$ ) between  $v_{IN}$  and  $v_{OUT1}$ ? What is the small signal gain ( $A_{v2}$ ) between  $v_{OUT1}$  and  $v_{OUT2}$ ? Using  $A_{v1}$  and  $A_{v2}$ , find the overall gain ( $A_{v,tot}$ ) between  $v_{IN}$  and  $v_{OUT2}$ . Attach the SPICE netlist to the end of this prelab.

$A_{v1} =$

$A_{v2} =$

$A_{v,tot} =$